
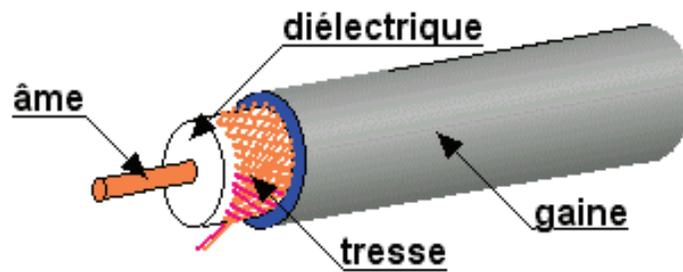


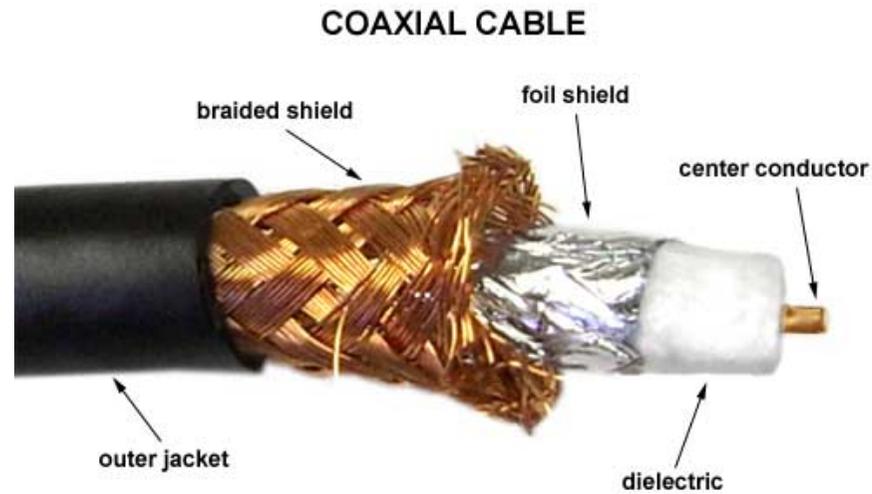Propagation in coaxial transmission lines



Connectors

Les connecteurs présentent une grande variété de formes et de tailles. En plus de types standard, les connecteurs peuvent être de **polarité inverse** (sexes inversés) ou de **filetée inverse**.



MC-Card



MMCX



RP-MMCX



U.FL



SMA Male



RPSMA Male



SMA Female



RPSMA Female



TNC Male



RPTNC Male



TNC Female



RPTNC Female



N-Male



N-Female

Adaptators and Pigtails

Les adaptateurs et pigtails sont utilisés pour interconnecter les différents types de câbles ou de dispositifs.



SMA female to N male



N male to N male



N female to N female



SMA male to TNC male



U.FL to RP-TNC
male pigtail



U.FL to N male pigtail




SMA male to N female

Losses

La perte (ou **atténuation**) d'un câble coaxial dépend de la construction du câble et la fréquence de fonctionnement. Le montant total de la perte est proportionnelle à la longueur du câble.

type de cable	diametre	atténuation à 2.4 GHz	atténuation à 5.3 GHz
RG-58	4.95 mm	0.846 dB/m	1.472 dB/m
RG-213	10.29 mm	0.475 dB/m	0.829 dB/m
LMR-400	10.29 mm	0.217 dB/m	0.341 dB/m
LDF4-50A	16 mm	0.118 dB/m	0.187 dB/m


1. Problem statement

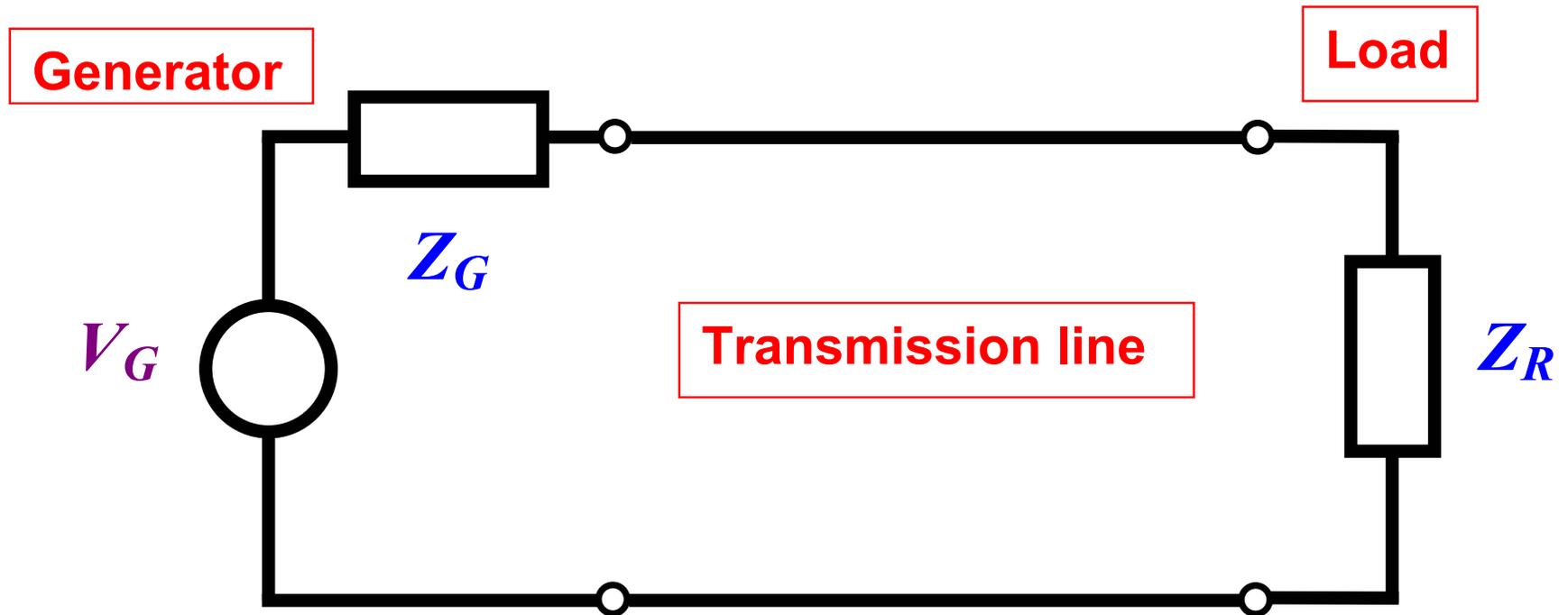

Outline

1. Problem Statement
2. Looking for a equivalent network
3. Propagation in a line
4. Maximal power transmission
5. Transient propagation (case studies)

Case I: $L \ll \lambda$

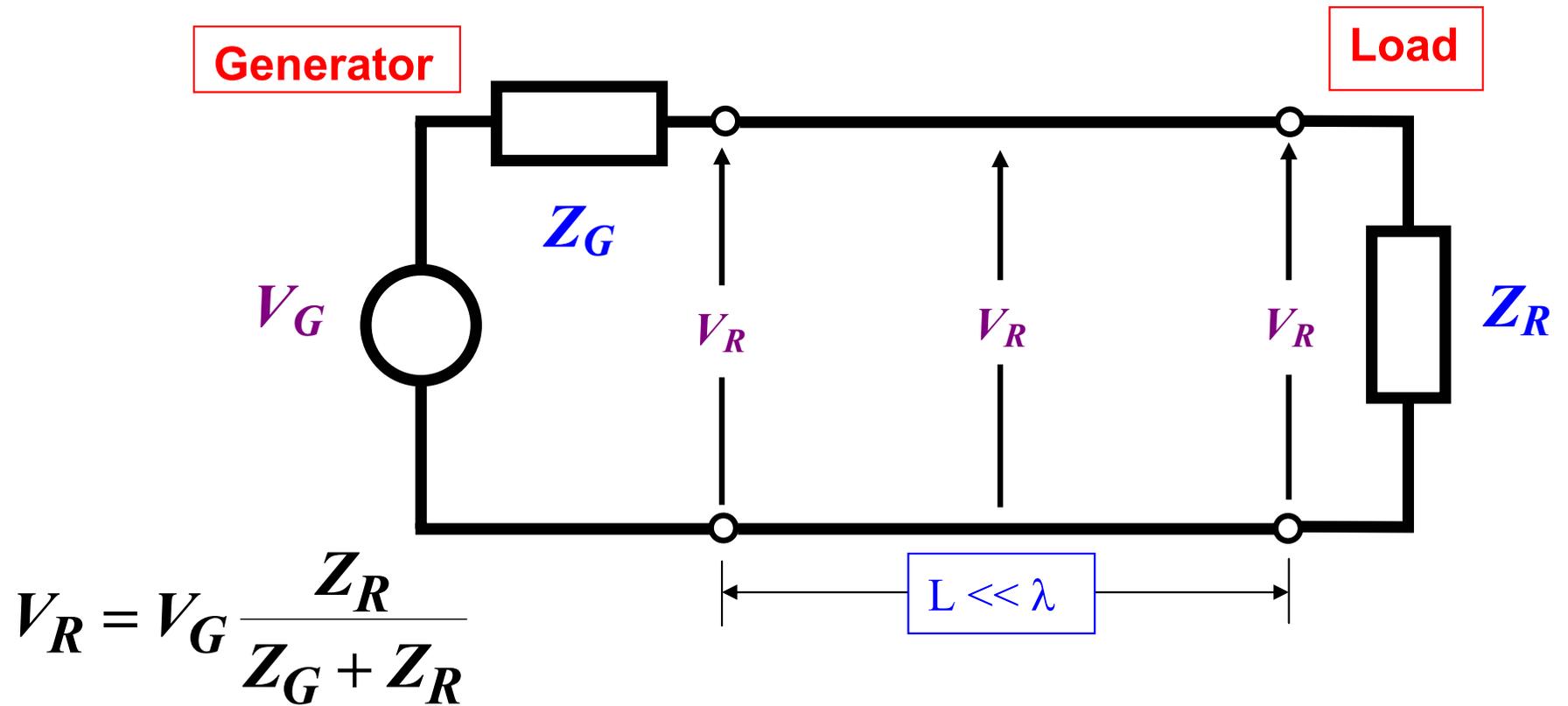

Orders of magnitudes

Let's look at some examples. The electricity supplied to households consists of high power sinusoidal signals, with **frequency** of **60Hz** or **50Hz**, depending on the country. Assuming that the insulator between wires is air ($\epsilon \approx \epsilon_0$), the **wavelength** for 60Hz is:

$$\lambda = \frac{c}{f} = \frac{2.999 \times 10^8}{60} \approx 5.0 \times 10^6 \text{ m} = 5,000 \text{ km}$$

which is the about the **distance between S. Francisco and Boston!**


Let's compare to a **frequency** in the microwave range, for instance **60 GHz**. The **wavelength** is given by

$$\lambda = \frac{c}{f} = \frac{2.999 \times 10^8}{60 \times 10^9} \approx 5.0 \times 10^{-3} \text{ m} = 5.0 \text{ mm}$$


which is comparable to the **size of a microprocessor chip.**

Which conclusions do you draw?

Case 2 : $L \gg \lambda$


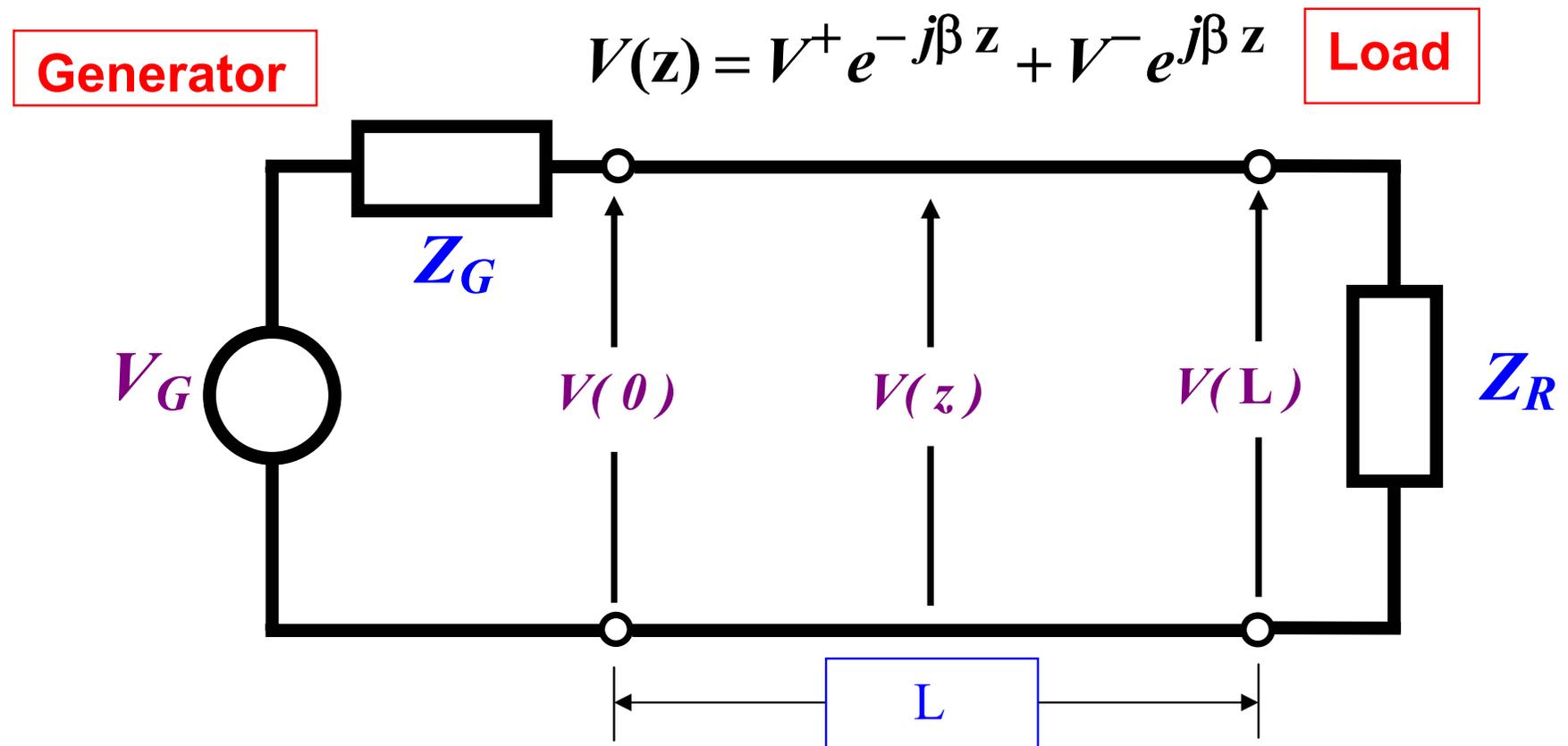


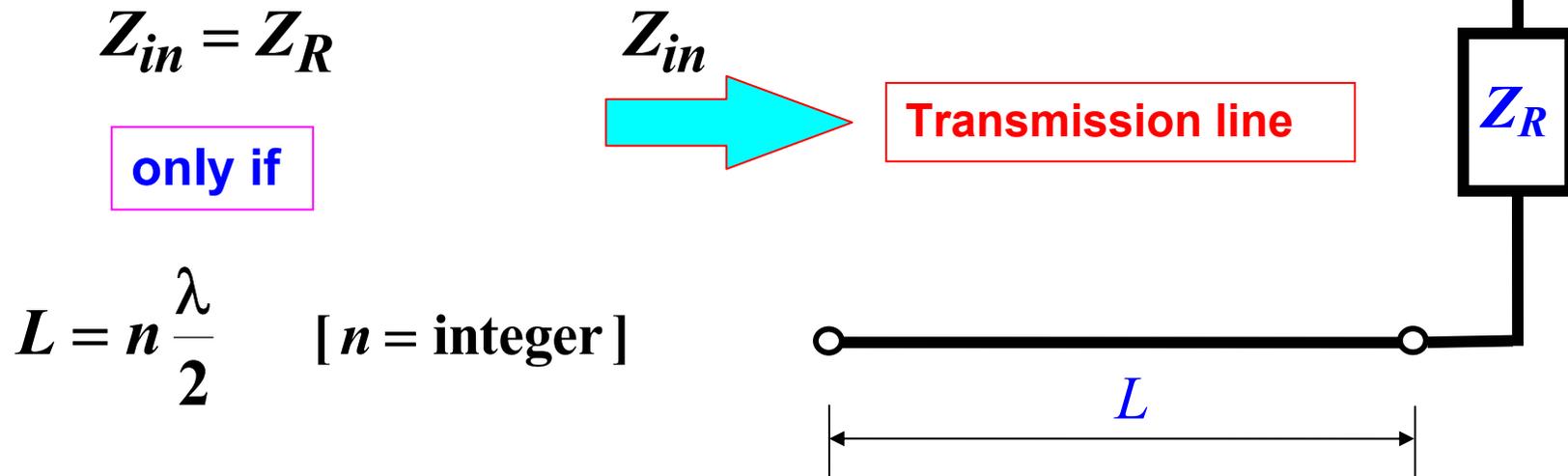The simplest circuit problem that we can study consists of a voltage **generator** connected to a **load** through a **uniform transmission line**. In general, the impedance seen by the generator is not the same as the impedance of the load, because of the presence of the transmission line, except for some very particular cases:




Our first goal is to determine the **equivalent impedance** seen by the generator, that is, the input impedance of a line terminated by the load. Once that is known, standard circuit theory can be used.

2. Looking for an equivalent network

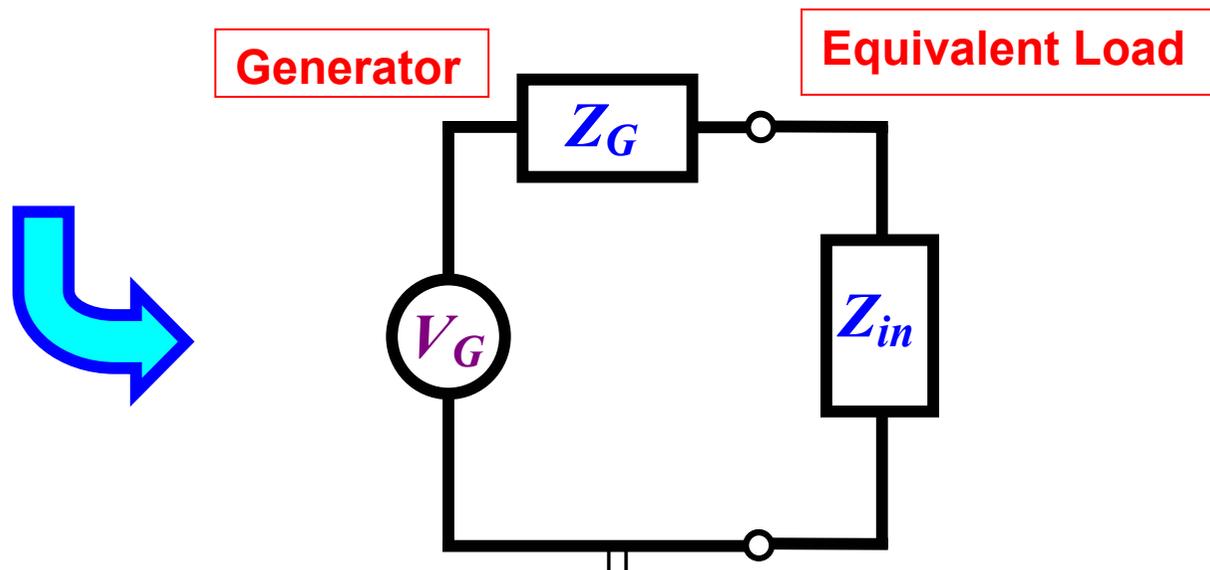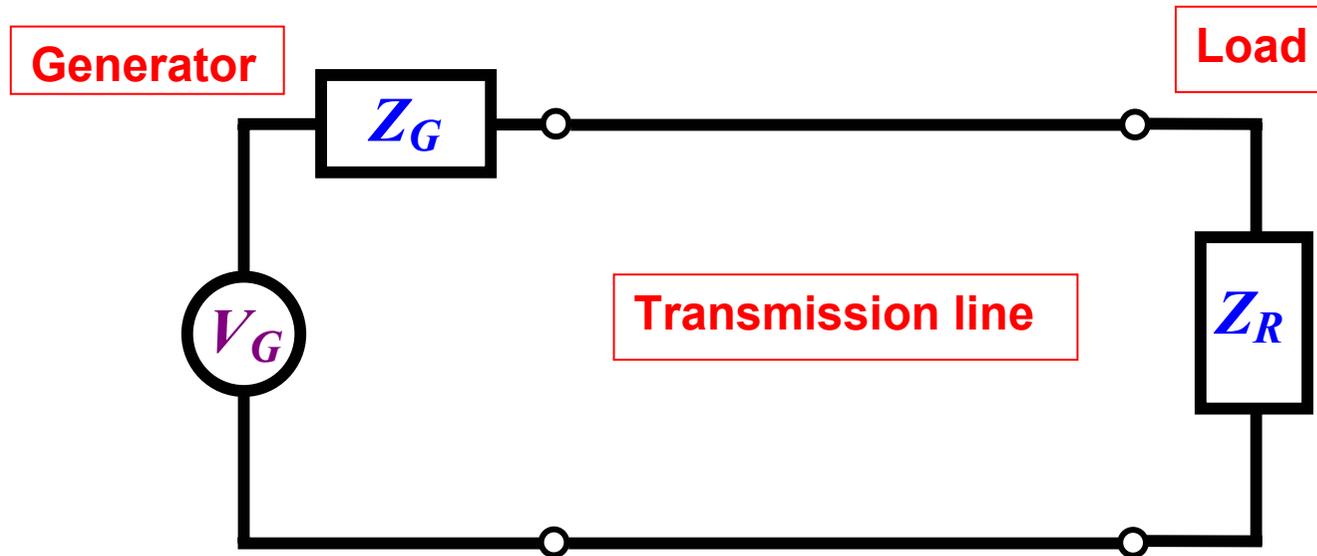

Line equivalent network

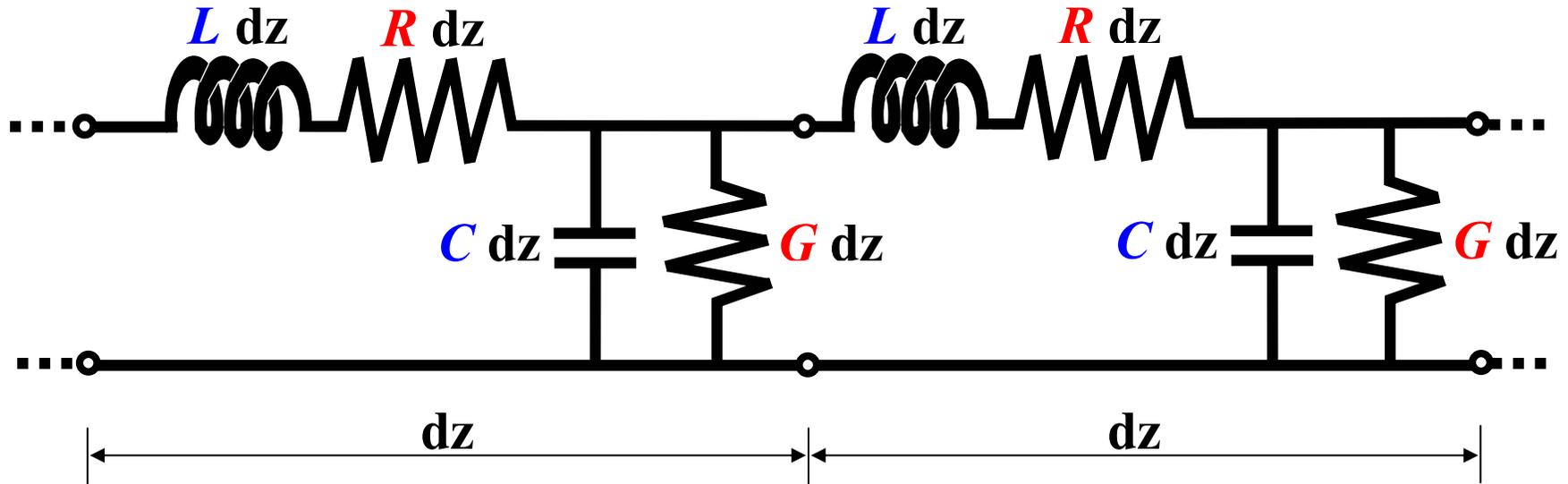

The impedance parameters L , R , C , and G represent:

L = series inductance per unit length


R = series resistance per unit length

C = shunt capacitance per unit length

G = shunt conductance per unit length.

Each cell of the distributed circuit will have impedance elements with values: Ldz , Rdz , Cdz , and Gdz , where dz is the infinitesimal length of the cells.

Without losses

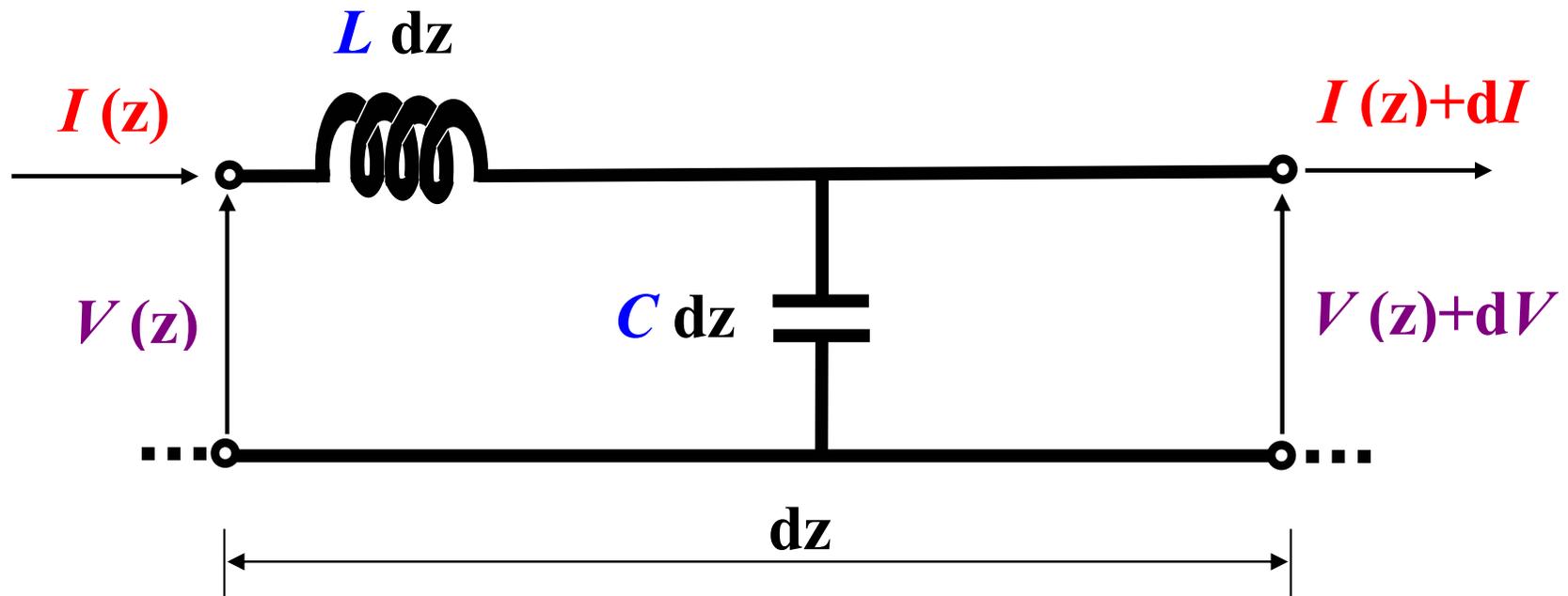

Signal propagation is quantified in terms of the solution of the so-called Telegrapher's equations

$$\frac{dI}{dz} = -j\omega C V$$

$$\frac{d^2 V}{dz^2} = -j\omega L \frac{dI}{dz} = j\omega L j\omega C V = -\omega^2 LC V$$

$$\frac{d^2 I}{dz^2} = -j\omega C \frac{dV}{dz} = j\omega C j\omega L I = -\omega^2 LC I$$

$$\frac{dV}{dz} = -j\omega L I$$

The general solution for the **voltage** equation is

$$V(\mathbf{z}) = V^+ e^{-j\beta \mathbf{z}} + V^- e^{j\beta \mathbf{z}}$$

where the **wave propagation constant** is

$$\beta = \omega \sqrt{LC}$$

We have the following useful relations:

$$\begin{aligned}\beta &= \frac{2\pi}{\lambda} = \frac{2\pi f}{v_p} = \frac{\omega}{v_p} \\ &= \frac{\omega \sqrt{\epsilon_r \mu_r}}{c} = \omega \sqrt{\epsilon_0 \mu_0} \sqrt{\epsilon_r \mu_r} = \omega \sqrt{\epsilon \mu}\end{aligned}$$

Here, $\lambda = v_p / f$ is the **wavelength** of the dielectric medium surrounding the conductors of the transmission line and

$$v_p = \frac{1}{\sqrt{\epsilon_0 \epsilon_r \mu_0 \mu_r}} = \frac{1}{\sqrt{\epsilon \mu}}$$

is the **phase velocity** of an electromagnetic wave in the dielectric.

As you can see, the propagation constant β can be written in many different, equivalent ways.

The **current** distribution on the transmission line can be readily obtained by **differentiation** of the result for the **voltage**

$$\frac{dV}{dz} = -j\beta V^+ e^{-j\beta z} + j\beta V^- e^{j\beta z} = -j\omega L I$$

which gives


$$I(z) = \sqrt{\frac{C}{L}} \left(V^+ e^{-j\beta z} - V^- e^{j\beta z} \right) = \frac{1}{Z_0} \left(V^+ e^{-j\beta z} - V^- e^{j\beta z} \right)$$

The **real** quantity

$$Z_0 = \sqrt{\frac{L}{C}}$$

is the “**characteristic impedance**” of the **loss-less transmission line**.

With losses

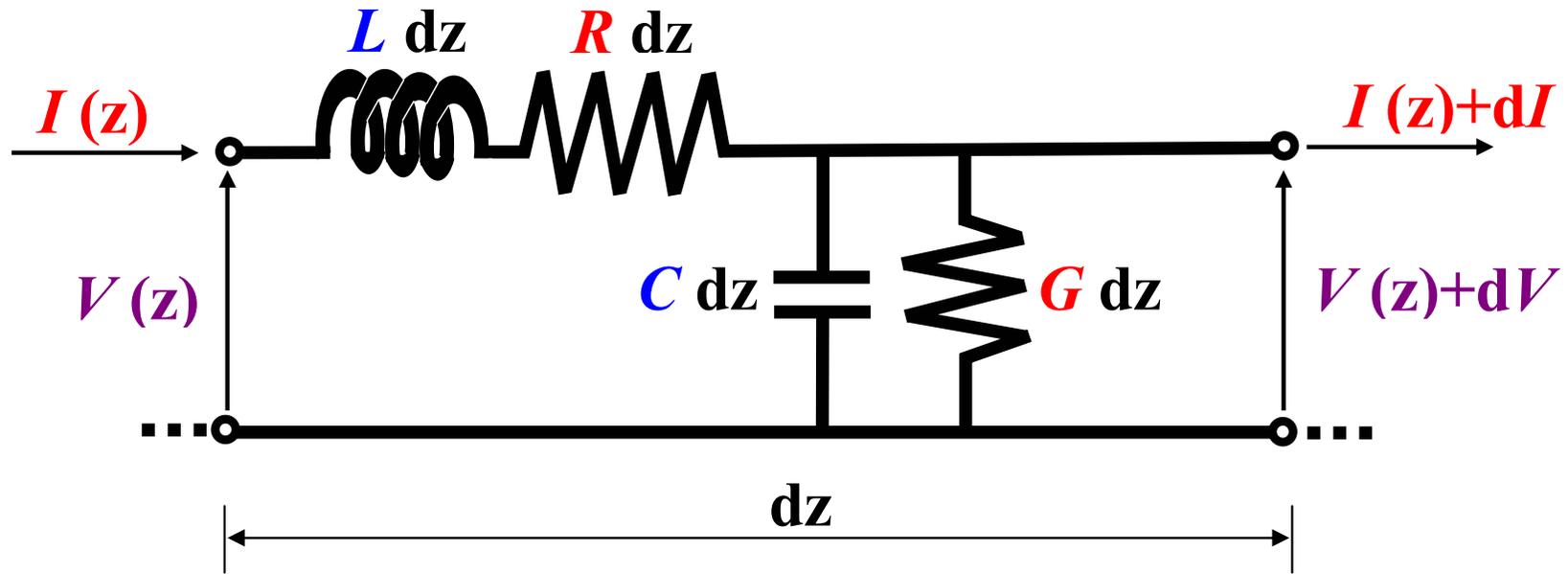

Telegrapher's equations with losses

$$\frac{dI}{dz} = -(j\omega C + G)V$$

$$\frac{d^2V}{dz^2} = -(j\omega L + R)\frac{dI}{dz} = (j\omega L + R)(j\omega C + G)V$$

$$\frac{d^2I}{dz^2} = -(j\omega C + G)\frac{dV}{dz} = (j\omega C + G)(j\omega L + R)I$$

$$\frac{dV}{dz} = -(j\omega L + R)I$$

with the “characteristic impedance” of the lossy transmission line

$$Z_0 = \sqrt{\frac{j\omega L + R}{j\omega C + G}}$$

Note: the characteristic impedance is now complex !

Common mistakes


For both loss-less and lossy transmission lines

the characteristic impedance does not depend on the line length

but only on the **metal** of the conductors, the **dielectric material** surrounding the conductors and the **geometry** of the line cross-section, which determine L , R , C , and G .

One must be careful not to interpret the characteristic impedance as some lumped impedance that can replace the transmission line in an equivalent circuit.

This is a very common mistake!

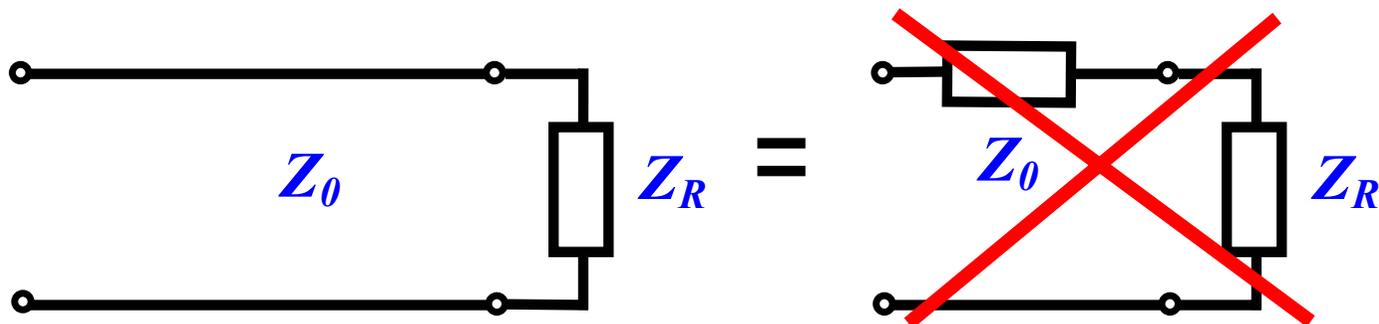

3. Propagation in a line

We have obtained the following solutions for the **steady-state voltage** and **current phasors** in a transmission line:



Loss-less line

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$
$$I(z) = \frac{1}{Z_0} \left(V^+ e^{-j\beta z} - V^- e^{j\beta z} \right)$$


Lossy line

$$V(z) = V^+ e^{-\gamma z} + V^- e^{\gamma z}$$
$$I(z) = \frac{1}{Z_0} \left(V^+ e^{-\gamma z} - V^- e^{\gamma z} \right)$$

General case

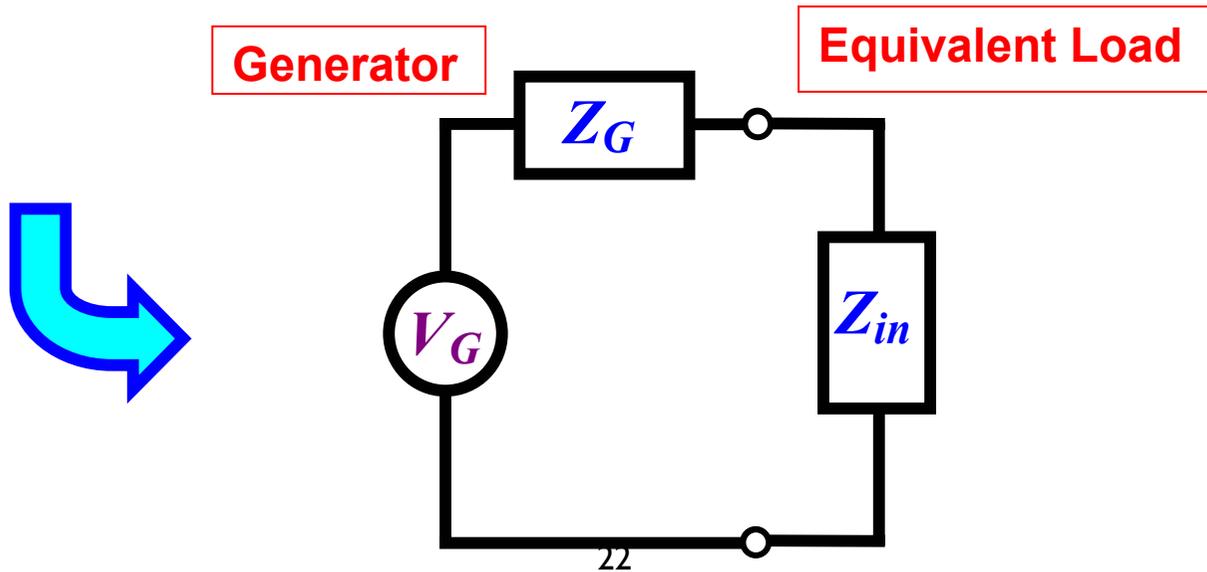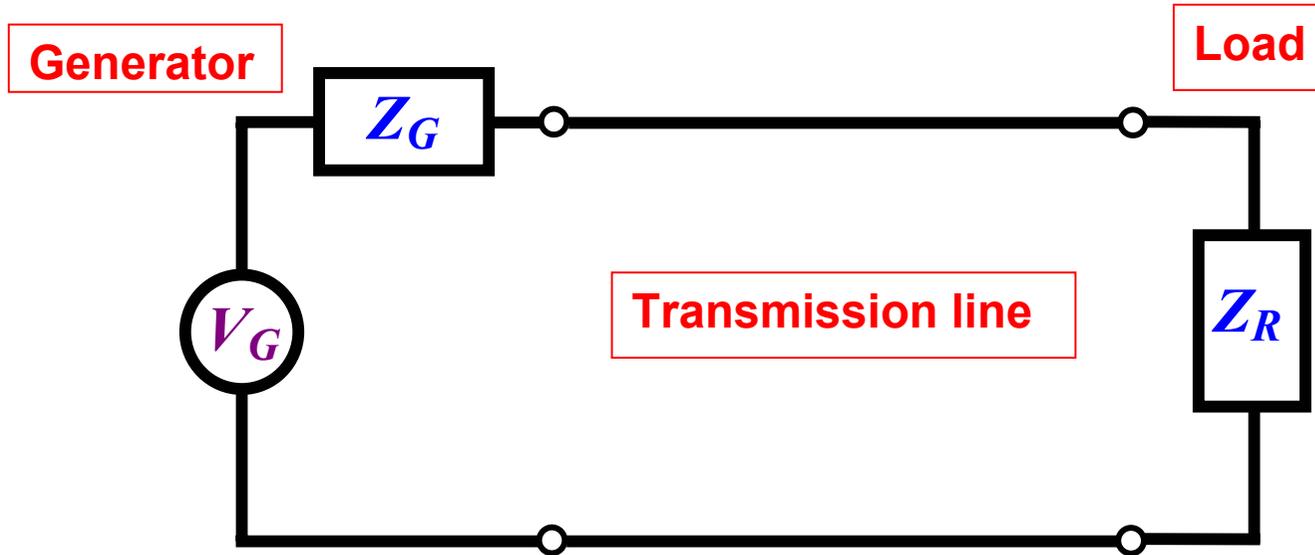

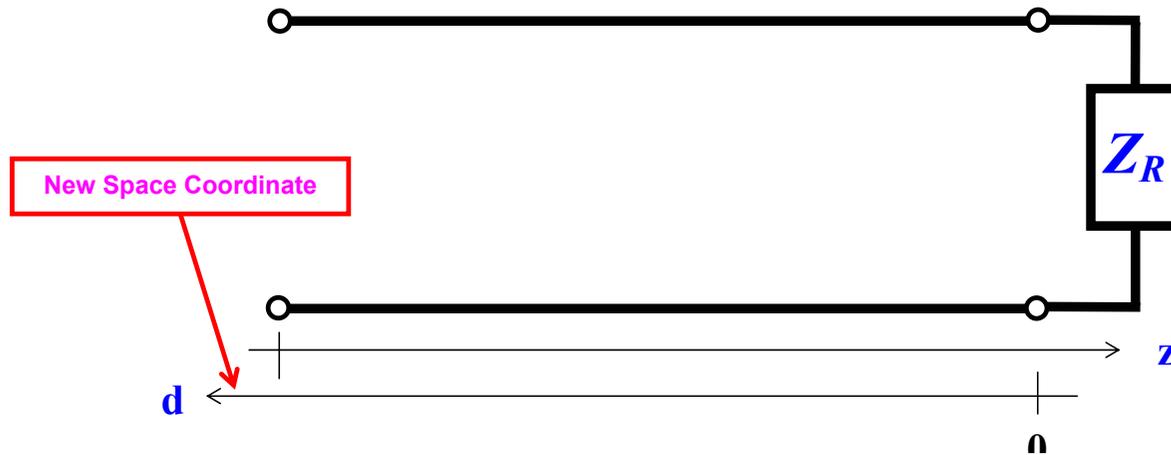Before we consider the boundary conditions, it is very convenient to shift the reference of the space coordinate so that the **zero reference is at the location of the load** instead of the generator. Since the analysis of the transmission line normally starts from the load itself, this will simplify considerably the problem later.



We adopt a new coordinate $d = -z$, with zero reference at the load location. The **new equations** for voltage and current along the lossy transmission line are

Loss-less line

$$V(d) = V^+ e^{j\beta d} + V^- e^{-j\beta d}$$

$$I(d) = \frac{1}{Z_0} (V^+ e^{j\beta d} - V^- e^{-j\beta d})$$

Lossy line

$$V(d) = V^+ e^{\gamma d} + V^- e^{-\gamma d}$$

$$I(d) = \frac{1}{Z_0} (V^+ e^{\gamma d} - V^- e^{-\gamma d})$$

At the **load** ($d = 0$) we have, for both cases,

$$V(0) = V^+ + V^-$$
$$I(0) = \frac{1}{Z_0} (V^+ - V^-)$$

For a given load impedance Z_R , the **load boundary condition** is

$$V(0) = Z_R I(0)$$

Therefore, we have

$$V^+ + V^- = \frac{Z_R}{Z_0} (V^+ - V^-)$$

from which we obtain the **voltage load reflection coefficient**

$$\Gamma_R = \frac{V^-}{V^+} = \frac{Z_R - Z_0}{Z_R + Z_0}$$

We can introduce this result into the transmission line equations as

Loss-less line

$$V(d) = V^+ e^{j\beta d} \left(1 + \Gamma_R e^{-2j\beta d} \right)$$
$$I(d) = \frac{V^+ e^{j\beta d}}{Z_0} \left(1 - \Gamma_R e^{-2j\beta d} \right)$$

Lossy line

$$V(d) = V^+ e^{\gamma d} \left(1 + \Gamma_R e^{-2\gamma d} \right)$$
$$I(d) = \frac{V^+ e^{\gamma d}}{Z_0} \left(1 - \Gamma_R e^{-2\gamma d} \right)$$

At each line location we define a **Generalized Reflection Coefficient**

$$\Gamma(d) = \Gamma_R e^{-2j\beta d}$$

$$\Gamma(d) = \Gamma_R e^{-2\gamma d}$$

and the line equations become


$$V(d) = V^+ e^{j\beta d} (1 + \Gamma(d))$$
$$I(d) = \frac{V^+ e^{j\beta d}}{Z_0} (1 - \Gamma(d))$$

$$V(d) = V^+ e^{\gamma d} (1 + \Gamma(d))$$
$$I(d) = \frac{V^+ e^{\gamma d}}{Z_0} (1 - \Gamma(d))$$

We define the **line impedance** as

$$Z(d) = \frac{V(d)}{I(d)} = Z_0 \frac{1 + \Gamma(d)}{1 - \Gamma(d)}$$

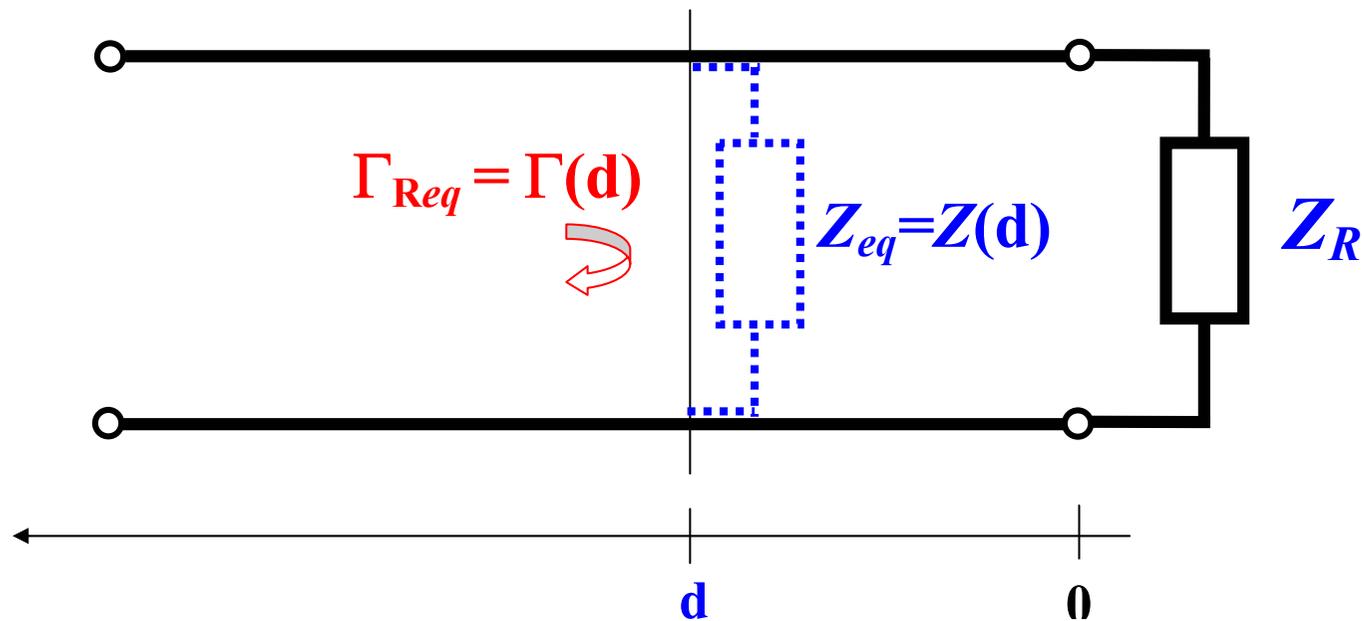A simple circuit diagram can illustrate the significance of line impedance and generalized reflection coefficient:



If you imagine to **cut** the line at location **d**, the input impedance of the portion of line terminated by the load is the same as the line impedance at that location **“before the cut”**. The behavior of the line on the **left** of location **d** is the same if an equivalent impedance with value **Z(d)** replaces the cut out portion. The reflection coefficient of the new load is equal to **Γ(d)**

$$\Gamma_{Req} = \Gamma(d) = \frac{Z_{Req} - Z_0}{Z_{Req} + Z_0}$$

If the total length of the line is **L**, the input impedance is obtained from the formula for the line impedance as

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{V(L)}{I(L)} = Z_0 \frac{1 + \Gamma(L)}{1 - \Gamma(L)}$$

The input impedance is the **equivalent impedance** representing the entire line terminated by the load.

The **characteristic impedance** of the **low-loss line** is a **real** quantity for all practical purposes and it is approximately the same as in a corresponding **loss-less line**

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \approx \sqrt{\frac{L}{C}}$$

and the **phase velocity** associated to the wave propagation is

$$v_p = \frac{\omega}{\beta} \approx \frac{1}{\sqrt{LC}}$$

BUT NOTE:

In the case of the low-loss line, the equations for voltage and current retain the same form obtained for general lossy lines.

Again, we obtain the **loss-less transmission line** if we assume

$$R = 0 \qquad G = 0$$

This is often acceptable in relatively short transmission lines, where the overall attenuation is small.

As shown earlier, the characteristic impedance in a loss-less line is exactly real

$$Z_0 = \sqrt{\frac{L}{C}}$$

while the propagation constant has no attenuation term

$$\gamma = \sqrt{(j\omega L)(j\omega C)} = j\omega \sqrt{LC} = j\beta$$

The loss-less line does not dissipate power, because $\alpha = 0$.

For all cases, the line impedance was defined as

$$Z(d) = \frac{V(d)}{I(d)} = Z_0 \frac{1 + \Gamma(d)}{1 - \Gamma(d)}$$

By including the appropriate generalized reflection coefficient, we can derive alternative expressions of the line impedance:


A) Loss-less line

$$Z(d) = Z_0 \frac{1 + \Gamma_R e^{-2j\beta d}}{1 - \Gamma_R e^{-2j\beta d}} = Z_0 \frac{Z_R + jZ_0 \tan(\beta d)}{jZ_R \tan(\beta d) + Z_0}$$

B) Lossy line (including low-loss)

$$Z(d) = Z_0 \frac{1 + \Gamma_R e^{-2\gamma d}}{1 - \Gamma_R e^{-2\gamma d}} = Z_0 \frac{Z_R + Z_0 \tanh(\gamma d)}{Z_R \tanh(\gamma d) + Z_0}$$

4. Maximal power transmission

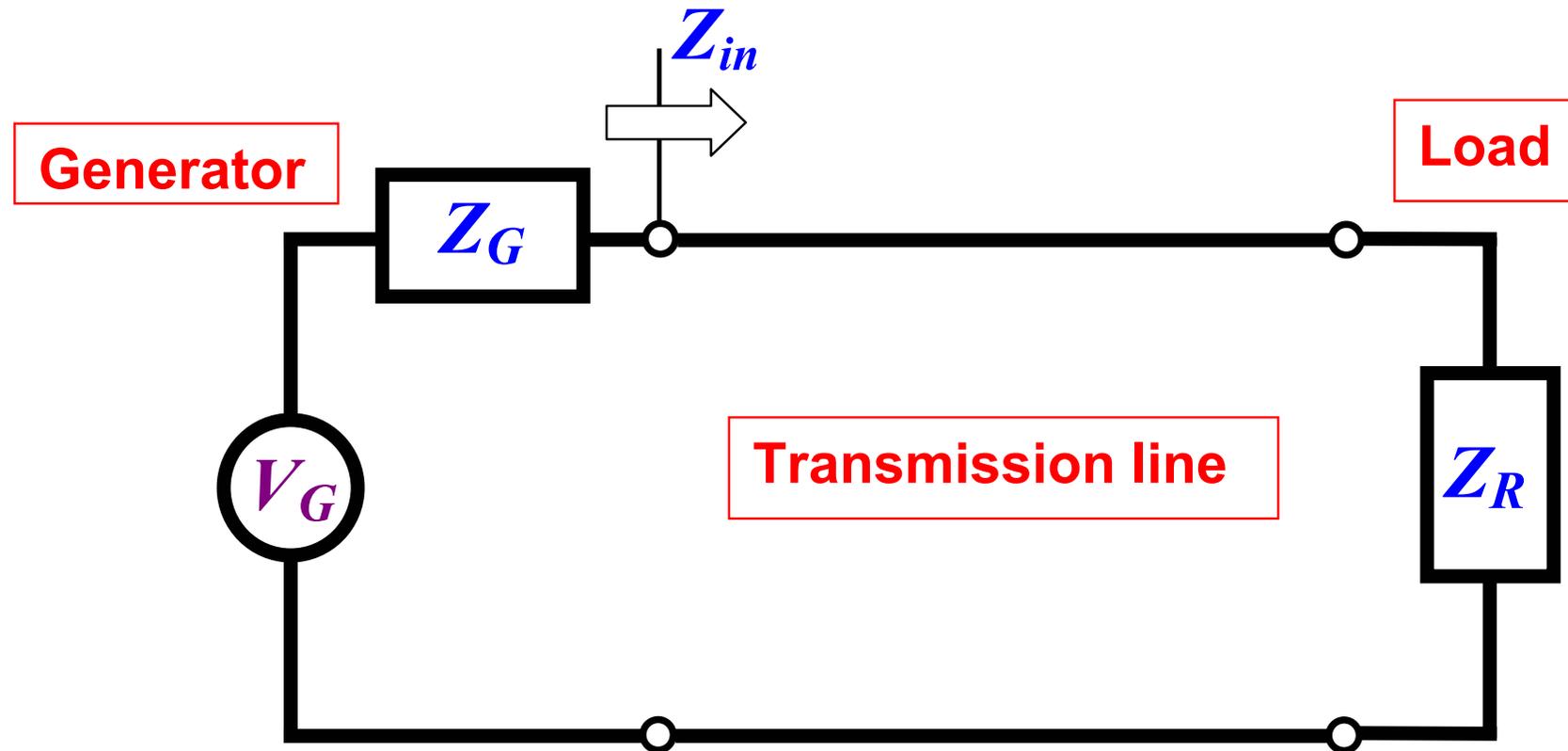

$$Z_G = Z_{in}^* \text{ for maximum power transfer}$$


The characteristic impedance of the **loss-less line** is **real** and we can express the power flow, anywhere on the line, as

$$\begin{aligned}
 \langle P(d, t) \rangle &= \frac{1}{2} \operatorname{Re}\{ V(d) I^*(d) \} \\
 &= \frac{1}{2} \operatorname{Re} \left\{ V^+ e^{j\beta d} \left(1 + \Gamma_R e^{-j2\beta d} \right) \right. \\
 &\quad \left. \frac{1}{Z_0} (V^+)^* e^{-j\beta d} \left(1 - \Gamma_R e^{-j2\beta d} \right)^* \right\} \\
 &= \underbrace{\frac{1}{2Z_0} |V^+|^2}_{\text{Incident wave}} - \underbrace{\frac{1}{2Z_0} |V^+|^2 |\Gamma_R|^2}_{\text{Reflected wave}}
 \end{aligned}$$

This result is valid for any location, including the input and the load, since the transmission line does not absorb any power.

Particular cases

$Z_R \rightarrow 0$ (SHORT CIRCUIT)

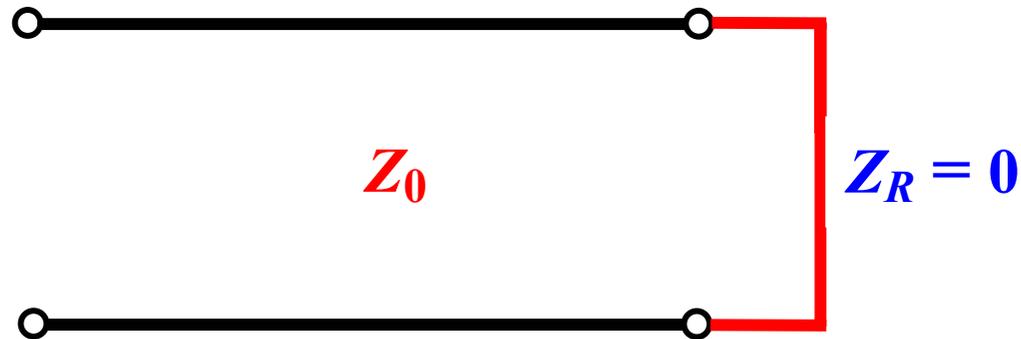

The load **boundary condition** due to the short circuit is $V(0) = 0$

$$\Rightarrow V(d = 0) = V^+ e^{j\beta 0} (1 + \Gamma_R e^{-j2\beta 0})$$

$$= V^+ (1 + \Gamma_R) = 0$$

$$\Rightarrow \Gamma_R = -1$$

Particular cases

$$Z_R \rightarrow \infty \text{ (OPEN CIRCUIT)}$$



$$Z_0$$

$$Z_R \rightarrow \infty$$



The load **boundary condition** due to the open circuit is $I(0) = 0$


$$\Rightarrow I(d = 0) = \frac{V^+}{Z_0} e^{j\beta 0} (1 - \Gamma_R e^{-j2\beta 0})$$

$$= \frac{V^+}{Z_0} (1 - \Gamma_R) = 0$$

$$\Rightarrow \Gamma_R = 1$$

Particular cases

$$Z_R = Z_0 \text{ (MATCHED LOAD)}$$

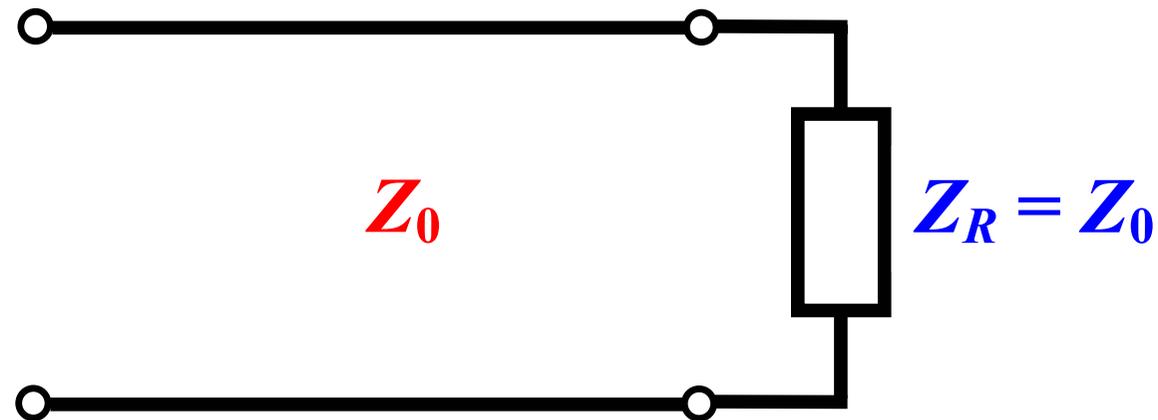

The **reflection coefficient** for a matched load is

$$\Gamma_R = \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{Z_0 - Z_0}{Z_0 + Z_0} = 0$$

no reflection!

Particular cases

Short circuited transmission line – Fixed frequency

L ↓	$L = 0$	$Z_{in} = 0$	short circuit	}
	$0 < L < \frac{\lambda}{4}$	$\text{Im}\{Z_{in}\} > 0$	inductance	
	$L = \frac{\lambda}{4}$	$Z_{in} \rightarrow \infty$	open circuit	
	$\frac{\lambda}{4} < L < \frac{\lambda}{2}$	$\text{Im}\{Z_{in}\} < 0$	capacitance	
	$L = \frac{\lambda}{2}$	$Z_{in} = 0$	short circuit	}
	$\frac{\lambda}{2} < L < \frac{3\lambda}{4}$	$\text{Im}\{Z_{in}\} > 0$	inductance	
	$L = \frac{3\lambda}{4}$	$Z_{in} \rightarrow \infty$	open circuit	
	$\frac{3\lambda}{4} < L < \lambda$	$\text{Im}\{Z_{in}\} < 0$	capacitance	

...


Particular cases

Open circuit transmission line – Fixed frequency

L 	$L = 0$	$Z_{in} \rightarrow \infty$	open circuit	}
	$0 < L < \frac{\lambda}{4}$	$\text{Im}\{Z_{in}\} < 0$	capacitance	
	$L = \frac{\lambda}{4}$	$Z_{in} = 0$	short circuit	
	$\frac{\lambda}{4} < L < \frac{\lambda}{2}$	$\text{Im}\{Z_{in}\} > 0$	inductance	
	$L = \frac{\lambda}{2}$	$Z_{in} \rightarrow \infty$	open circuit	}
	$\frac{\lambda}{2} < L < \frac{3\lambda}{4}$	$\text{Im}\{Z_{in}\} < 0$	capacitance	
	$L = \frac{3\lambda}{4}$	$Z_{in} = 0$	short circuit	
	$\frac{3\lambda}{4} < L < \lambda$	$\text{Im}\{Z_{in}\} > 0$	inductance	
...				

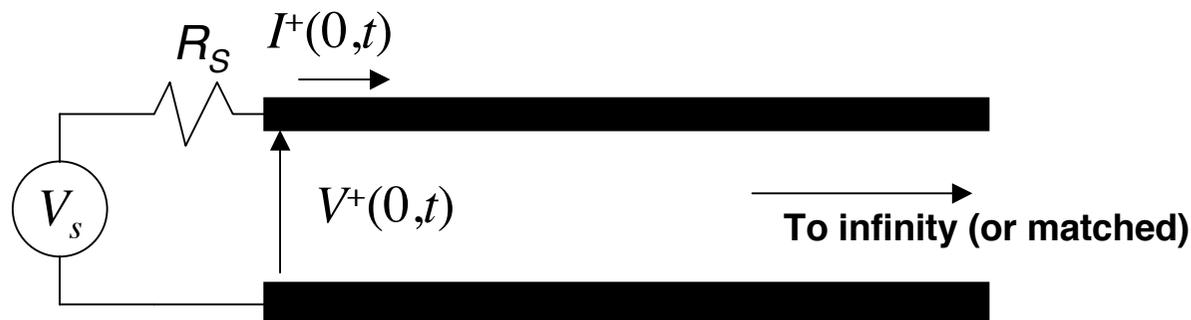
5. Transient propagation

The **characteristic impedance** dictates the amplitude of the voltage waveform launched on the line



$$\left. \begin{aligned} V_s(t) &= V^+(0,t) + I^+(0,t)R_s \\ V^+(0,t) &= Z_0 I^+(0,t) \end{aligned} \right\} \Rightarrow V^+(0,t) = V_s(t) \frac{Z_0}{Z_0 + R_s}$$

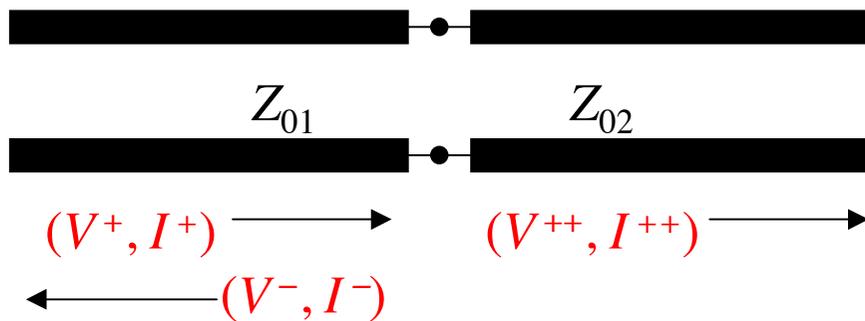Discontinuities in the characteristic impedance of a transmission line give rise to reflections



At the junction it is:

$$V_1 = V^+ + V^- = V_2 = V^{++}$$

$$I_1 = \frac{1}{Z_{01}}(V^+ - V^-) = I_2 = \frac{V^{++}}{Z_{02}}$$

$$\left. \begin{array}{l} V^- = \Gamma V^+ \\ I^- = -\frac{V^-}{Z_{01}} \end{array} \right\} \text{ and } \left. \begin{array}{l} V^{++} = T V^+ \\ I^{++} = \frac{V^{++}}{Z_{02}} \end{array} \right\}$$

$$\left. \begin{array}{l} \text{Reflection Coefficient: } \Gamma = \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}} \\ \text{Transmission Coefficient: } T = \frac{2Z_{02}}{Z_{02} + Z_{01}} \end{array} \right\}$$

Maintaining a fairly constant value of the characteristic impedance along an interconnect path is essential for reflection suppression.

Source and load impedances impact transmission line performance of the interconnect



Source reflection coefficient

$$\Gamma_S(f) = \frac{Z_S(f) - Z_0}{Z_S(f) + Z_0}$$


Load reflection coefficient:

$$\Gamma_L(f) = \frac{Z_L(f) - Z_0}{Z_L(f) + Z_0}$$

Load transmission coefficient:

$$T_L(f) = 1 + \Gamma_L(f) = \frac{2Z_L(f)}{Z_L(f) + Z_0}$$

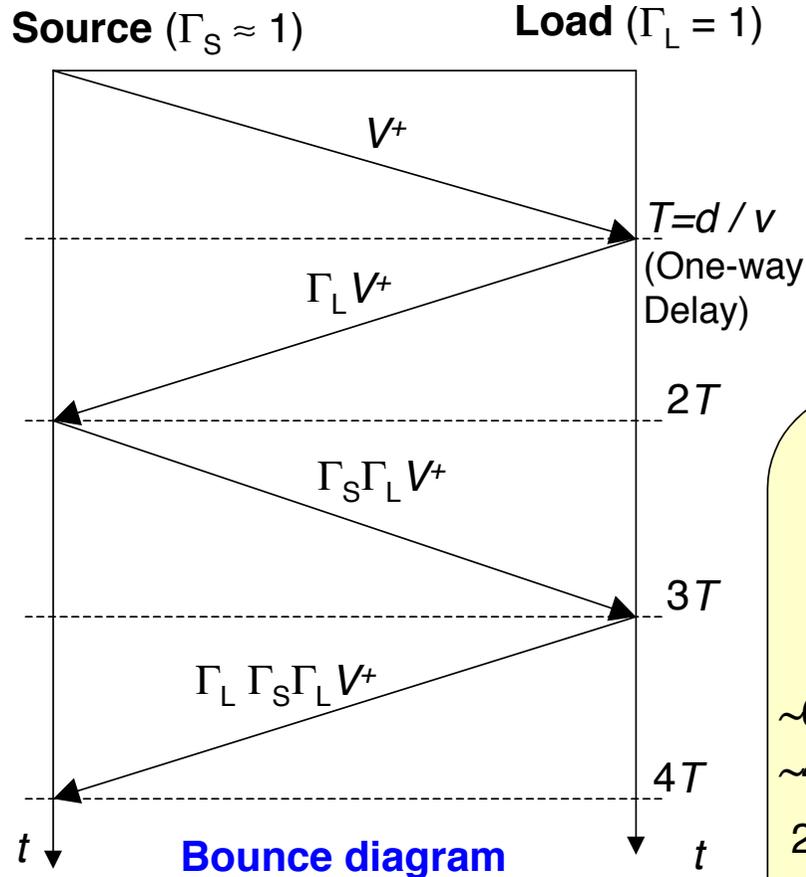
Example: Unterminated interconnect ($Z_L = \infty$) driven by high source impedance driver with $Z_S \gg Z_0$ (e.g. unbuffered CMOS)



Excitation: Step Pulse of amplitude V_0

$$V^+ = V_0 \frac{Z_0}{Z_S + Z_0} \ll V_0, \quad \Gamma_S = \frac{Z_S - Z_0}{Z_S + Z_0} \approx 1$$
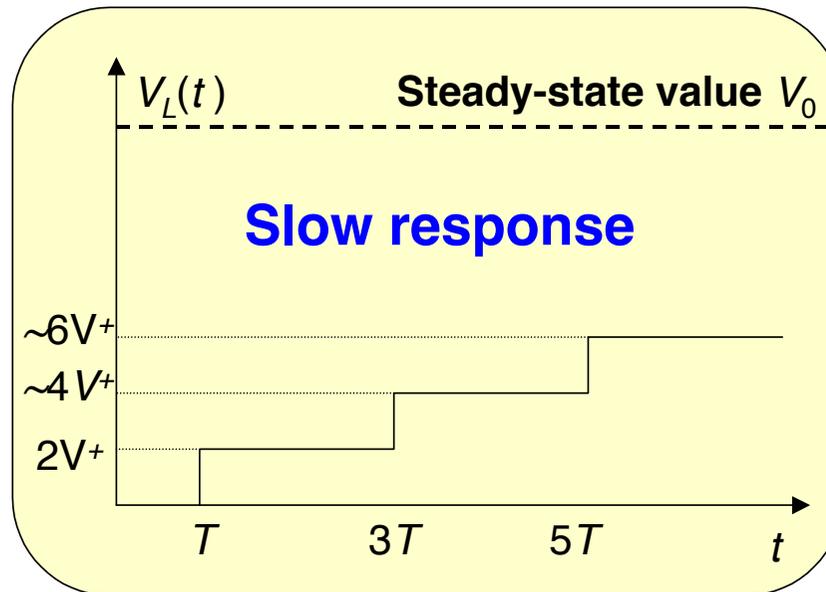
$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 1, \quad T_L = 2$$



Example: Unterminated interconnect ($Z_L = \infty$) driven by low source impedance driver with $Z_S < Z_0$ (e.g. ECL or strong TTL)

Source ($\Gamma_S \approx -1$)

Load ($\Gamma_L = 1$)

Excitation: Step Pulse of amplitude V_0 ; $Z_0 = 7Z_S$

$$V^+ = V_0 \frac{Z_0}{Z_S + Z_0} \approx \frac{7}{8} V_0, \quad \Gamma_S = \frac{Z_S - Z_0}{Z_S + Z_0} = -0.75$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 1, \quad T_L = 2$$

